

# Combinational Logic

1. Introduction.
2. Analysis and Design Procedure for Combinational Logic Circuits.
3. Types of Combinational Circuit.

# Introduction

1. Combinational Logic Circuits are circuits designed by using different types of logic gates.
2. A logic gate is a fundamental building block of any electronic circuit.
3. In other word **Combinational Logic Circuits are memoryless digital logic circuits** whose output at any instant in time depends only on the combination of its inputs.
4. Means these circuits do not make use of any memory or storage device.

# Introduction

The digital system consists of two types of circuits as –

- a) Combinational circuits**
- b) Sequential circuits**

# Introduction

Combinational circuit consists of logic gates whose output at any time is determined from the present combination of inputs. The logic gate is the most basic building block of combinational logic circuit.

A combinational circuit consists of:

- **Input variables**
- **Logic gates**
- **Output variables**

# Introduction

The function implemented by combinational circuit is depend upon the Boolean expressions. The combinational circuit having ‘n’ inputs and ‘m’ outputs. The ‘n’ number of inputs shows that there are  $2^n$  possible combinations of bits at the input.



# Introduction

At all combinational circuit can be designed by the following steps of design process- 3

1. Stated problem.
2. Ascertain the input and output variables.
3. The input and output variables are allocated letter symbols.
4. Construction of a truth table to encounter input -output requirements.
5. Writing Boolean expressions for numerous output variables in relations of input variables.

# Introduction

6. The basic Boolean expression is acquired by any method of minimization — algebraic, or tabulation method or Karnaugh map method.

7. A logic diagram is understood from the simplified Boolean expression using logic gates.

□ The logic gates are combined in such a way that the output state depends completely on the input states. Combinational logic circuits have no memory, timing or feedback loops, their operation is prompt. A combinational logic circuit performs an operation assigned logically by a Boolean expression or truth table.

# Introduction

- The logic gates are combined in such a way that the output state depends completely on the input states.
- Combinational logic circuits have no memory, timing or feedback loops, their operation is prompt. A combinational logic circuit performs an operation assigned logically by a Boolean expression or truth table.




# Introduction

- The **three main methods** of specifying the function of a combinational logic circuit as –
  1. **Boolean Algebra:** This forms the algebraic expression viewing the operation of the logic circuit for each input variable whichever True or False that results in a logic “1” output.
  2. **Truth Table:** A truth table expresses the function of a logic gate by providing a brief list that **shows all the output** states in tabular form for each possible combination of input variable that the gate could meet.

# Introduction

**3. Logic Diagram:** This is a graphical representation of a logic circuit that displays the wiring and connections of each individual logic gate, signified by a specific graphical symbol that implements the logic circuit.

# Classification of Combinational Logic

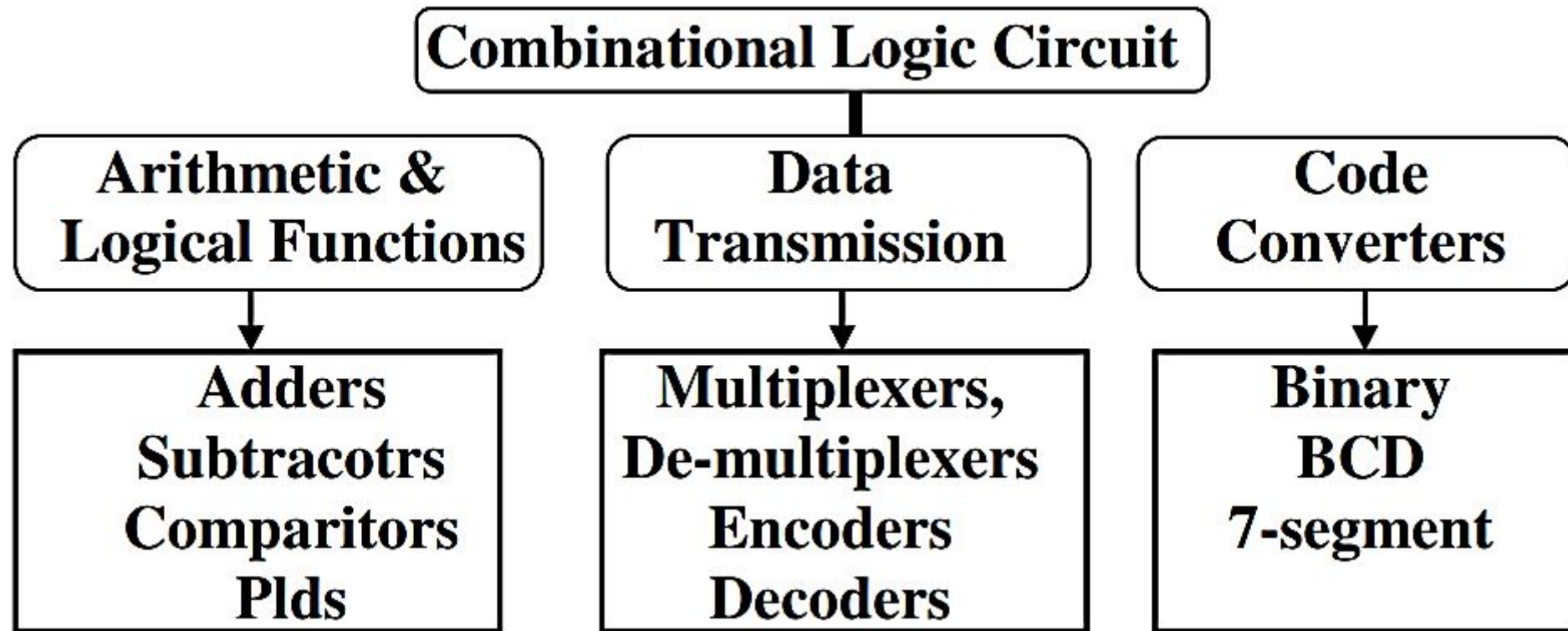


# Classification of Combinational Logic

One of the greatest uses of combinational logic is in **Multiplexer and De-multiplexer** type circuits. Here, multiple inputs or outputs are connected to a common signal stripe and logic gates are used to decode an address to select a single data input or output switch.
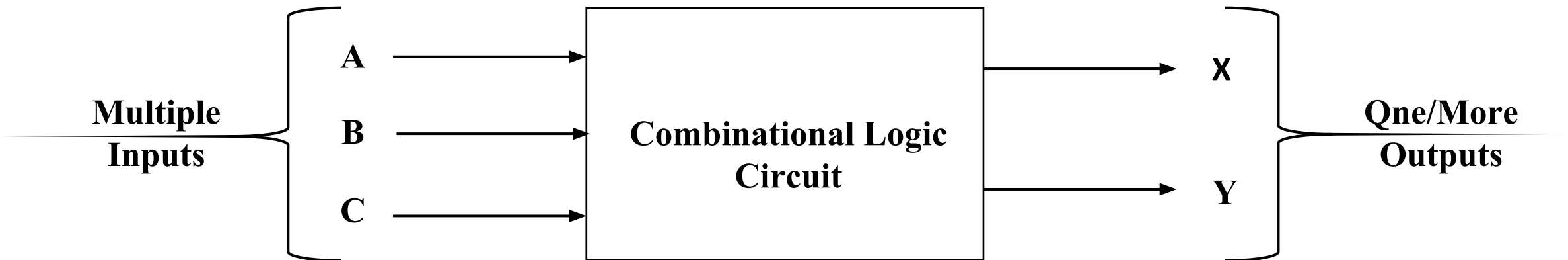
# Multiple Input Combinational Circuit

- Multi input gates can be made by constructing gates of the same type with fewer inputs. The figure below shown how a three input AND gate can be made out of two input AND gates. The same logical standard applies - the output goes “**low**” (0) if any of the inputs are made “**high**” (1).



# Multiple Input Combinational Circuit

- Combinational Logic Circuits are made up from basic logic **NAND**, **NOR** or **NOT gates** that are connected together to produce more complex switching circuits. These logic gates are the building blocks of combinational logic circuits.
- An example of a combinational circuit-
- Decoder, which converts the binary code data present at its input into a number of diverse output lines, one at a time producing an equivalent decimal code at its output.

# Multiple Input Combinational Circuit

- The number of possible input states is equal to two to the power of the number of inputs: 6

$$\text{Number of possible input states} = 2^n$$

Where,

$n$  = Number of inputs

- This increase in the number of possible input states obviously allows for more complex gate performance. Instead of simply inverting a single “high” or “low” logic level, the output of the gate will be determined by whatsoever combination of 1’s and 0’s is present at the input stations.

# Arithmetic Circuits – Basic Building Blocks

- **Half-Adder**

A half-adder is an arithmetic circuit block that can be used to add two bits. Such a circuit thus has two inputs that represent the two bits to be added and two outputs, with one producing the SUM output and the other producing the CARRY.

The truth table of a half-adder, showing all possible input combinations and the corresponding outputs. The Boolean expressions for the SUM and CARRY outputs are given by the equations



# Arithmetic Circuits – Basic Building Blocks

- Half-Adder

Inputs		Outputs	
<i>A</i>	<i>B</i>	<i>S</i>	<i>C</i>
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

# Arithmetic Circuits – Basic Building Blocks


- Half-Adder

$$\text{SUM } S = A'.B + A.B'$$

$$\text{CARRY } C = A.B$$

# Arithmetic Circuits – Basic Building Blocks

- Half-Adder

 

# Arithmetic Circuits – Basic Building Blocks

## ▪ Full-Adder

- A full adder circuit is an arithmetic circuit block that can be used to add three bits to produce a SUM and a CARRY output. Such a building block becomes a necessity when it comes to adding binary numbers with a large number of bits.
- The full adder circuit overcomes the limitation of the half-adder, which can be used to add two bits only. Let us recall the procedure for adding larger binary numbers.

# Arithmetic Circuits – Basic Building Blocks

- **Full-Adder**

- We begin with the addition of LSBs of the two numbers. We record the sum under the LSB column and take the carry, if any, forward to the next higher column bits.
- As a result, when we add the next adjacent higher column bits, we would be required to add three bits if there were a carry from the previous addition. We have a similar situation for the other higher column bits

# Arithmetic Circuits – Basic Building Blocks

## ▪ Full-Adder

Inputs			Outputs	
$A_n$	$B_n$	$C_{n-1}$	$S_n$	$C_n$
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

# Arithmetic Circuits – Basic Building Blocks


- Full-Adder

$$S = \overline{A}.\overline{B}.C_{\text{in}} + \overline{A}.B.\overline{C}_{\text{in}} + A.\overline{B}.\overline{C}_{\text{in}} + A.B.C_{\text{in}}$$

$$C_{\text{out}} = \overline{A}.B.C_{\text{in}} + A.\overline{B}.C_{\text{in}} + A.B.\overline{C}_{\text{in}} + A.B.C_{\text{in}}$$

# Arithmetic Circuits – Basic Building Blocks


- **Full-Adder**

 



# Arithmetic Circuits – Basic Building Blocks

- Full-Adder

 

# Arithmetic Circuits – Basic Building Blocks

- **Half-Subtractor**

A half-subtractor is a combinational circuit that can be used to subtract one binary digit from another to produce a DIFFERENCE output and a BORROW output. The BORROW output here specifies whether a ‘1’ has been borrowed to perform the subtraction.

# Arithmetic Circuits – Basic Building Blocks


Inputs		Outputs	
<i>A</i>	<i>B</i>	<i>D</i>	<i>C</i>
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

# Arithmetic Circuits – Basic Building Blocks

$$D = \bar{A}B + A\bar{B} = A \oplus B$$

$$C = \bar{A}B$$
 
# Arithmetic Circuits – Basic Building Blocks



# Arithmetic Circuits – Basic Building Blocks

## ▪ Full-Subtractor

A full subtractor performs subtraction operation on two bits, a minuend and a subtrahend, and also takes into consideration whether a '1' has already been borrowed by the previous adjacent lower minuend bit or not.

As a result, there are three bits to be handled at the input of a full subtractor, namely the two bits to be subtracted and a borrow bit designated as Bin.

# Arithmetic Circuits – Basic Building Blocks

- **Full-Subtractor**

There are two outputs, namely the DIFFERENCE output D and the BORROW output Bo. The BORROW output bit tells whether the minuend bit needs to borrow a ‘1’ from the next possible higher minuend bit.

# Arithmetic Circuits – Basic Building Blocks

Inputs			Outputs	
$A_n$	$B_n$	$C_{n-1}$	$D_n$	$C_n$
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1




# Arithmetic Circuits – Basic Building Blocks

- $$\begin{aligned} D &= A'B'C + A'BC' + AB'C' + ABC \\ &= A'(B'C + BC') + A(B'C' + BC) \\ &= A'(B \oplus C) + A(B \oplus C)' \\ D &= A \oplus B \oplus C \end{aligned}$$

$$\begin{aligned} B &= A'B'C + A'BC' + A'BC + ABC \\ &= A'(B'C + BC') + BC(A' + A) \\ B &= A'(B \oplus C) + BC \end{aligned}$$

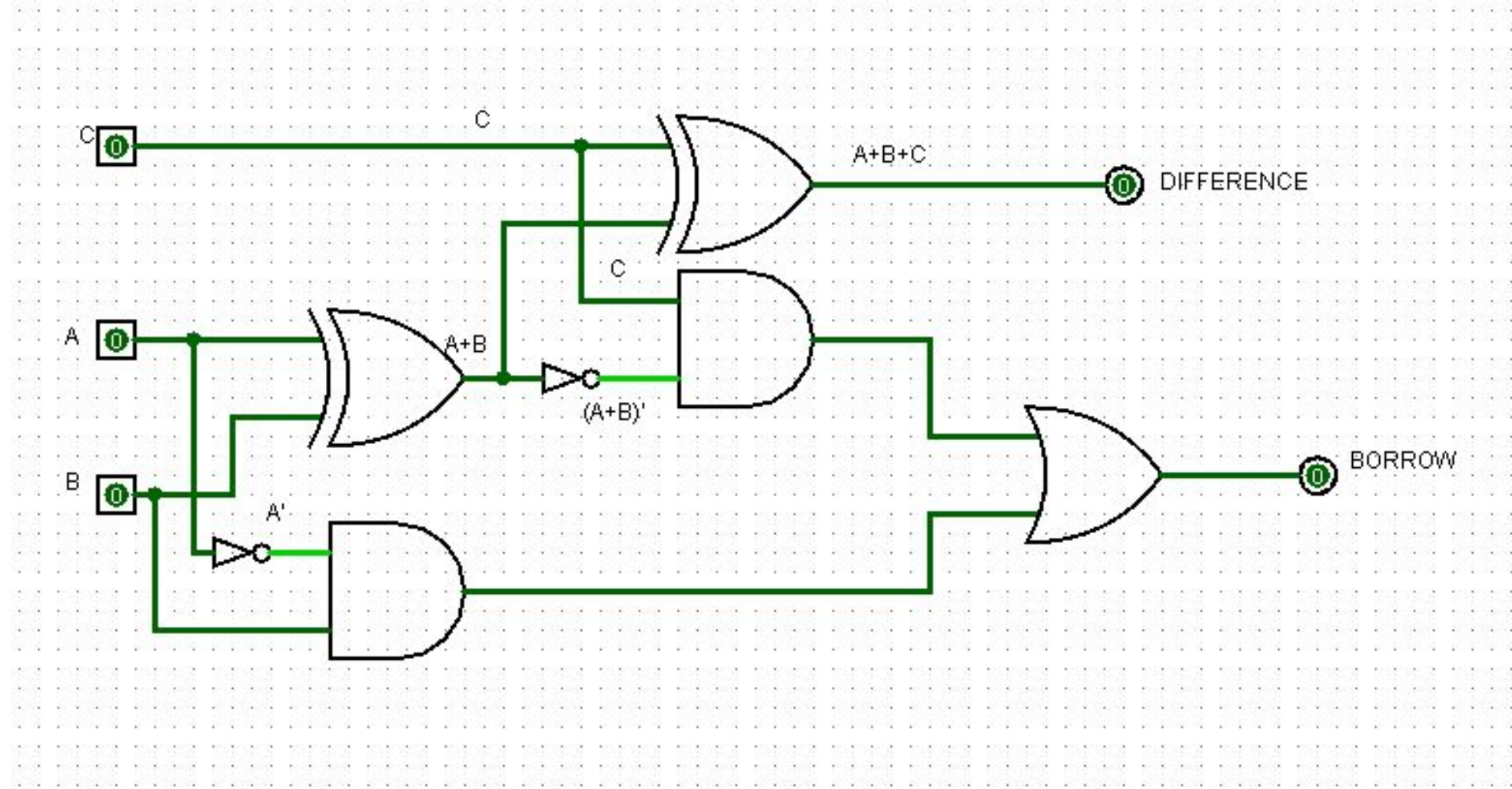
# Arithmetic Circuits – Basic Building Blocks



# Arithmetic Circuits – Four bit binary adder


- Each of the adders is composed of four full adders (FAs) connected in cascade. The block schematic arrangement of a four-bit adder is represented in next slide for reference and further discussion.
- This type of adder is also called a parallel binary adder because all the bits of the augend and addend are present and are fed to the full adder blocks simultaneously.
- Theoretically, the addition operation in various full adders takes place simultaneously.
 
# Arithmetic Circuits – Four bit binary adder



# Arithmetic Circuits – Four bit binary adder

- Each Full adder unit

 

# Arithmetic Circuits – Binary Multiplier


- Binary Multiplier is a combinational circuit that performs Binary Multiplication.
- Binary Multiplication is done in the same way as Decimal multiplication is done.
- Suppose  $15 * 13$

$$\begin{array}{r} 15 \\ 13 \\ \hline 45 \\ +15-- \\ \hline 195 \end{array}$$

# Arithmetic Circuits – Binary Multiplier

Multiplicand	Multiplier	Product
0	0	0
0	1	0
1	0	0
1	1	1
 
# Arithmetic Circuits – Binary Multiplier



$A_1 B_0$     $A_0 B_0$    -- Partial Products


$A_1 B_1$	$A_0 B_1$	--
<hr/>		
$P_2$	$P_1$	$P_0$



# Arithmetic Circuits – Binary Multiplier

1 0 0 1		Multiplicand	
× 1 1 0 1		Multiplier	
<hr/>			
1 0 0 1	} I	Partial Products	
0 0 0 0			II
1 0 0 1			III
1 0 0 1			IV
<hr/>			
1 1 1 0 1 0 1		Final Product	
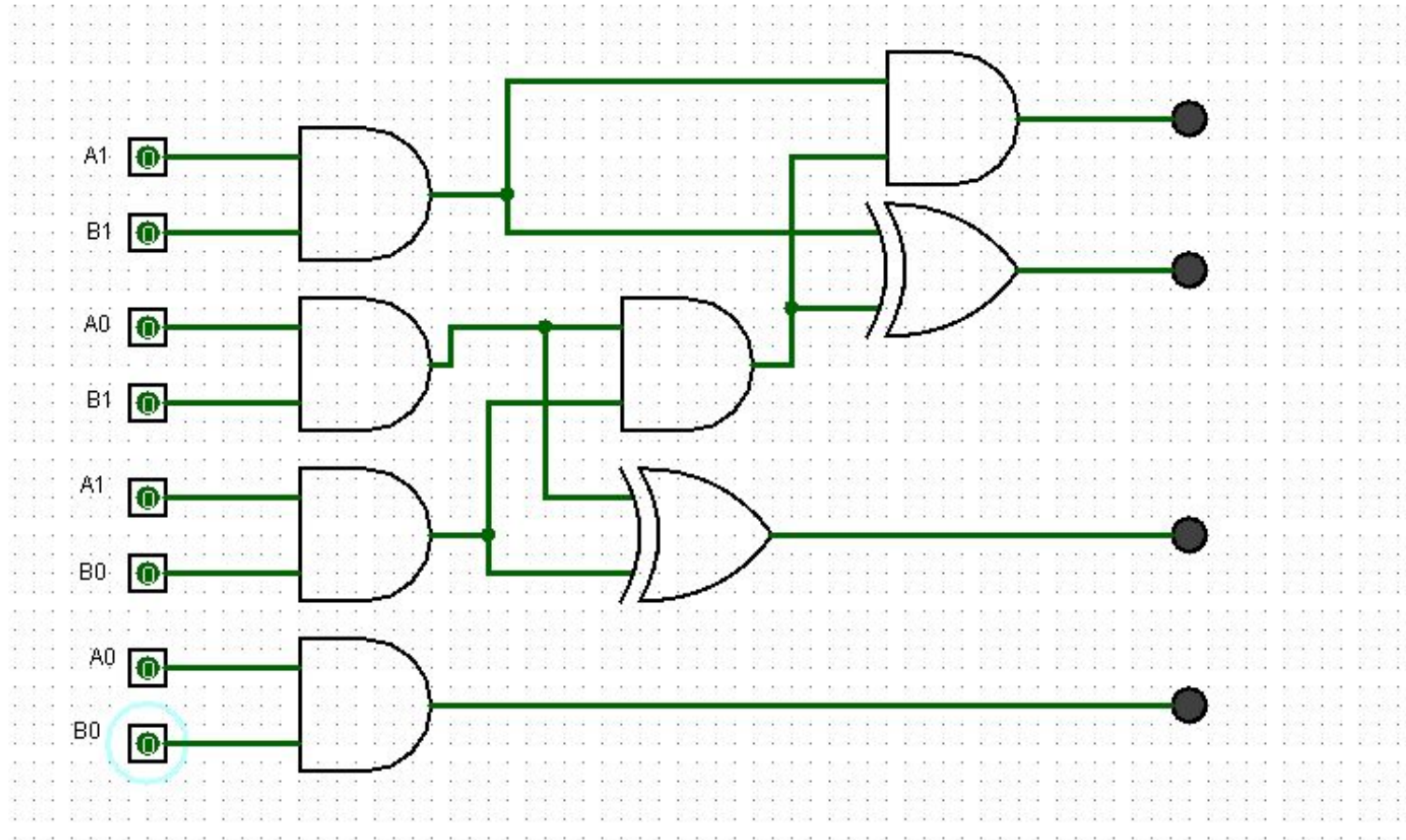
# Arithmetic Circuits – Binary Multiplier




# Arithmetic Circuits – 1's Complement OR 1-bit controlled Inverter

- A controlled inverter is needed when an adder is to be used as a subtractor.
- As outlined earlier, subtraction is nothing but addition of the 2's complement of the subtrahend to the minuend. Thus, the first step towards practical implementation of a subtractor is to determine the 2's complement of the subtrahend. And for this, one needs firstly to find 1's complement.
- A controlled inverter is used to find 1's complement. A one-bit controlled inverter is nothing but a two-input EX-OR gate with one of its inputs treated as a control input.

# Arithmetic Circuits – 1's Complement OR
 
## 1-bit controlled Inverter

- When the control input is LOW, the input bit is passed as such to the output. (Recall the truth table of an EX-OR gate.)
- When the control input is HIGH, the input bit gets complemented at the output.




# Arithmetic Circuits – Adder-Subtractor


- Subtraction of two binary numbers can be accomplished by adding 2's complement of the subtrahend to the minuend and disregarding the final carry, if any.
- If the MSB bit in the result of addition is a '0', then the result of addition is the correct answer.
- If the MSB bit is a '1', this implies that the answer has a negative sign. The true magnitude in this case is given by 2's complement of the result of addition.

# Arithmetic Circuits – Adder-Subtractor

- The control input here is referred to as the SUB input. When the SUB input is in logic '0' state, the four bits of the binary number (B3, B2, B1, B0) are passed on as such to the B inputs of the corresponding full adders.
- The outputs of the full adders in this case give the result of addition of the two numbers. When the SUB input is in logic '1' state, four bits of one of the numbers, (B3 B2 B1 B0) in the present case, get complemented.
- If the same '1' is also fed to the CARRY-IN of the LSB full adder, what we finally achieve is the addition of 2's complement and not 1's complement.

# Arithmetic Circuits – Adder-Subtractor

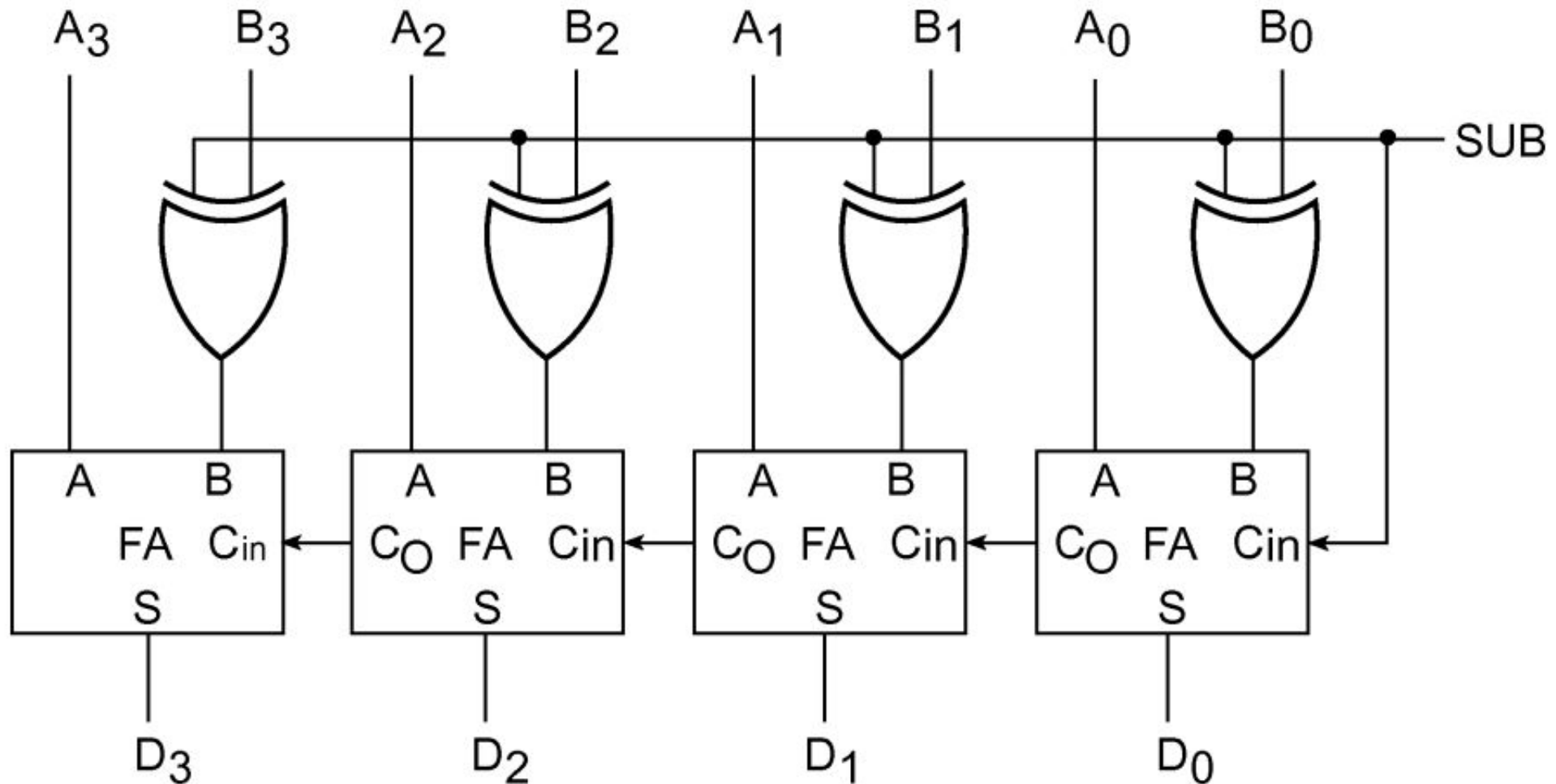

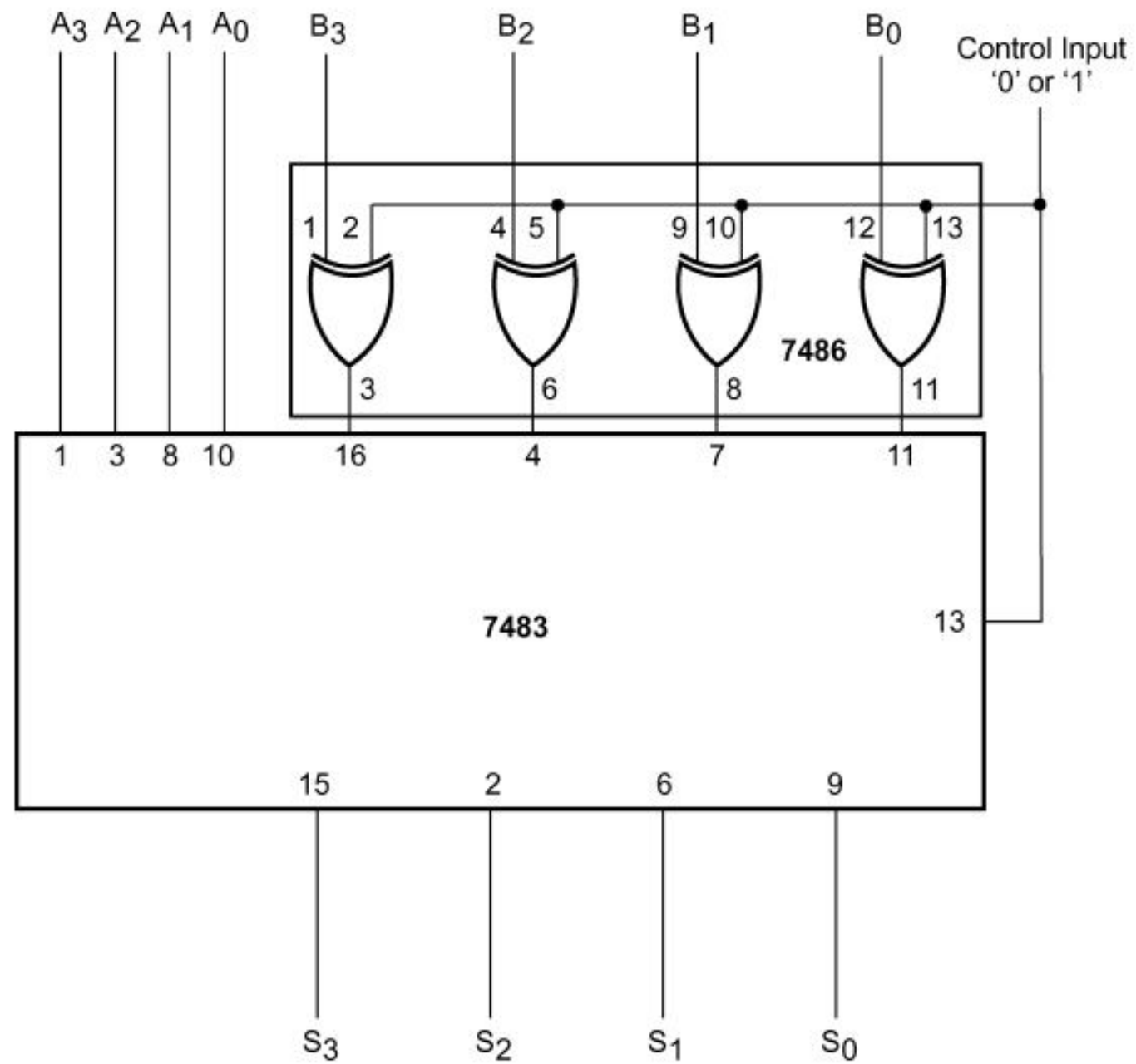



# BCD Adder

- A BCD adder is used to perform the addition of BCD numbers. A BCD digit can have any of the ten possible four-bit binary representations, that is, 0000, 0001, , 1001, the equivalent of decimal numbers 0, 1, ..... , 9.
- When we set out to add two BCD digits and we assume that there is an input carry too, the highest binary number that we can get is the equivalent of decimal number 19 (9 + 9 + 1). A BCD adder is used to perform the addition of BCD numbers.


# BCD Adder

- A BCD digit can have any of the ten possible four-bit binary representations, that is, 0000, 0001, ..... , 1001, the equivalent of decimal numbers 0, 1,..... , 9. When we set out to add two BCD digits and we assume that there is an input carry too, the highest binary number that we can get is the equivalent of decimal number 19 ( $9 + 9 + 1$ ).


# BCD Adder

Decimal sum	Binary sum					BCD sum				
	K	Z <sub>3</sub>	Z <sub>2</sub>	Z <sub>1</sub>	Z <sub>0</sub>	C	S <sub>3</sub>	S <sub>2</sub>	S <sub>1</sub>	S <sub>0</sub>
0	0	0	0	0	0	0	0	0	0	0
1	0	0	0	0	1	0	0	0	0	1
2	0	0	0	1	0	0	0	0	1	0
3	0	0	0	1	1	0	0	0	1	1
4	0	0	1	0	0	0	0	1	0	0
5	0	0	1	0	1	0	0	1	0	1
6	0	0	1	1	0	0	0	1	1	0
7	0	0	1	1	1	0	0	1	1	1
8	0	1	0	0	0	0	1	0	0	0
9	0	1	0	0	1	0	1	0	0	1
10	0	1	0	1	0	1	0	0	0	0
11	0	1	0	1	1	1	0	0	0	1
12	0	1	1	0	0	1	0	0	1	0
13	0	1	1	0	1	1	0	0	1	1
14	0	1	1	1	0	1	0	1	0	0
15	0	1	1	1	1	1	0	1	0	1
16	1	0	0	0	0	1	0	1	1	0
17	1	0	0	0	1	1	0	1	1	1
18	1	0	0	1	0	1	1	0	0	0
19	1	0	0	1	1	1	1	0	0	1

# BCD Adder

 

# BCD Adder

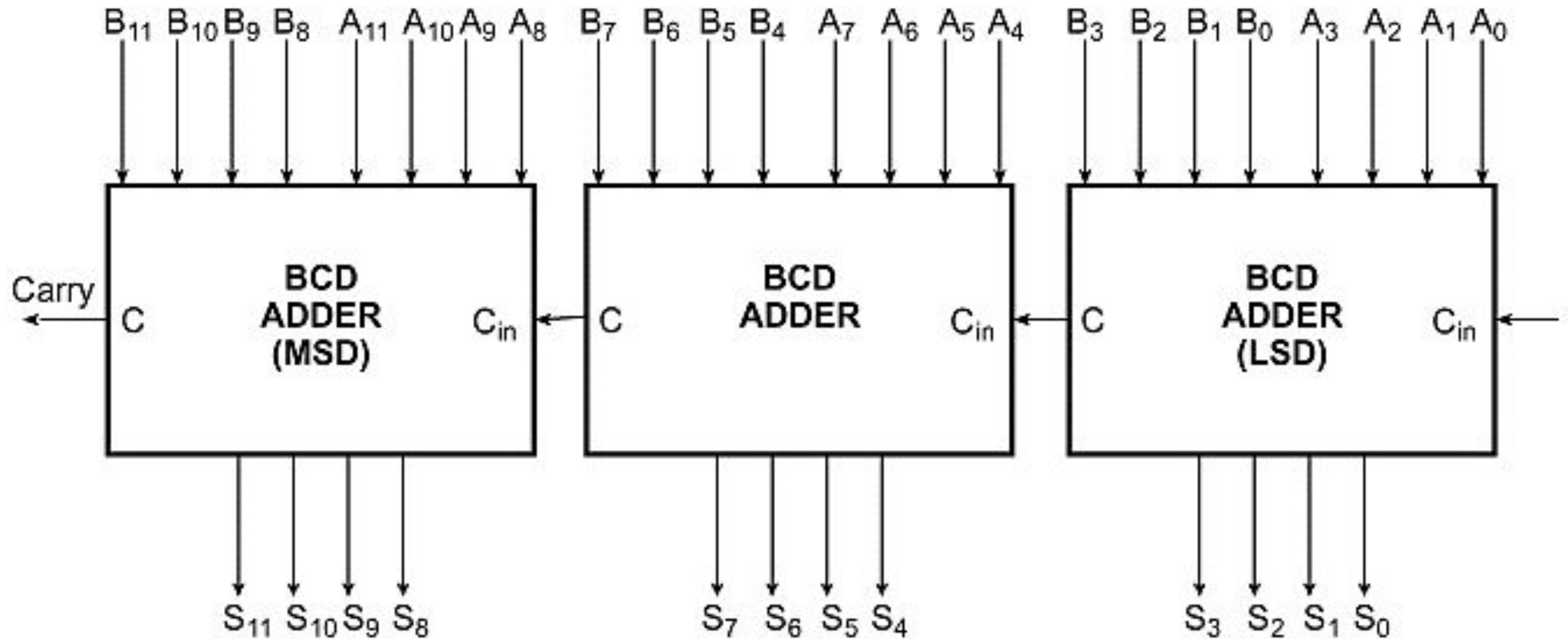


# Encoder

- An encoder is a digital circuit that achieves the inverse operation of a decoder. Therefore, the opposite of the decoding process is called encoding. An encoder is a combinational circuit that converts binary information from  $2^n$  input lines to a maximum of 'n' exclusive output lines.
 
# Encoder

- It has  $2^n$  input lines, only one “1” is active at any time and ‘n’ output lines. It encodes one active inputs to a coded binary output with ‘n’ bits. In an encoder, the number of outputs is less than the number of inputs.




# Encoder

Inputs								Outputs		
D <sub>0</sub>	D <sub>1</sub>	D <sub>2</sub>	D <sub>3</sub>	D <sub>4</sub>	D <sub>5</sub>	D <sub>6</sub>	D <sub>7</sub>	A	B	C
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1




# Encoder

 
 
# Decoder

- A decoder is a combinational circuit that converts binary information from 'n' input lines to a maximum of " $2^n$ " unique output lines.




# Decoder

- The encoded information is presented as 'n' inputs producing " $2^n$ " possible outputs. The " $2^n$ " output values are from 0 through " $2^n - 1$ ".
- A decoder is provided with enable inputs to activate decoded output based on data inputs. When any one enable input is unasserted, all outputs of decoder are disabled.

# Decoder

Inputs			Outputs							
A	B	C	Y <sub>0</sub>	Y <sub>1</sub>	Y <sub>2</sub>	Y <sub>3</sub>	Y <sub>4</sub>	Y <sub>5</sub>	Y <sub>6</sub>	Y <sub>7</sub>
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

# Decoder

 


# Multiplexer (Data Selector)

- A multiplexer or MUX, is a combinational circuit with more than one input line, one output line and more than one selection line.
- A multiplexer selects binary information present from one of many input lines, depending upon the logic status of the selection inputs, and directs it to the output line.
- Generally, there are “ $2^n$ ” input lines and  $n$  selection lines whose bit combinations determine which input is selected.

 
# Multiplexer (Data Selector)

- The multiplexer is labelled as MUX in block diagrams. A multiplexer is also called a data selector, since it selects one of many inputs and leads the binary information to the output line.


 
# Multiplexer (Data Selector) – 2-to-1 line Multiplexer

- This circuit has two data input lines, one output line and one selection line. When  $S = 0$ , the upper AND gate is enabled and  $I_0$  has a path to the output.
- When  $S = 1$ , the lower AND gate is enabled and  $I_1$  has a path to the output





# Multiplexer (Data Selector) – 2-to-1 line Multiplexer

- The multiplexer acts like an electronic switch that selects one of the two sources.

S	Y
0	$I_0$
1	$I_1$

# Multiplexer (Data Selector) –


## 4-to-1 line Multiplexer

- A 4-to-1-line multiplexer has four ( $2^n$ ) input lines, two ( $n$ ) select lines and one output line.
- It is the multiplexer comprising of four input channels and information of one of the station can be selected and transmitted to an output line according to the select inputs combinations.
- Selection of one of the four input station is possible by two selection inputs.
- Each of the four inputs  $I_0$  through  $I_3$ , is applied to one input of AND gate. Selection lines  $S_1$  and  $S_0$  are decoded to select a particular AND gate. The outputs of the AND gate are applied to a single OR gate that provides the 1-line output.

# Multiplexer (Data Selector) – 4-to-1 line Multiplexer

$S_1$	$S_0$	$Y$
0	0	$I_0$
0	1	$I_1$
1	0	$I_2$
1	1	$I_3$

 
# Multiplexer (Data Selector) – 4-to-1 line Multiplexer



$$Y = I_0 S_1' S_0' + I_1 S_1' S_0 + I_2 S_1 S_0' + I_3 S_1 S_0$$
 
# Demultiplexer

- Demultiplex means one into many. Demultiplexing is the process of taking information from one input and transmitting the same over on of several outputs




# Demultiplexer

- A decoder is similar to a demultiplexer, with one exception-there is no data input.
- The only inputs are the Select signals.
- Decoder is a logic circuit that converts  $n$ -bit binary input code into  $m$  output lines.
- The decoders presented here are called  **$n$ -to- $m$**  line decoders where  **$m < 2^n$** .
- Each output line will be activated for only one of the possible combination of inputs.

# Demultiplexer –
 
## 1-to-4 line Demultiplexer

- A 1-to-4 demultiplexer has a single input,  $D_{in}$ , four outputs ( $Y_0$  to  $Y_3$ ) and two select inputs ( $S_1$  and  $S_0$ ).



# Demultiplexer –

## 1-to-4 line Demultiplexer

- The input variable  $D_{in}$  has a path to all four outputs, but the input information is directed to only one of the output lines. The truth table of the 1-to-4 demultiplexer is shown below.




# Demultiplexer –



## 1-to-4 line Demultiplexer

Enable	S <sub>1</sub>	S <sub>0</sub>	D <sub>in</sub>	Y <sub>0</sub>	Y <sub>1</sub>	Y <sub>2</sub>	Y <sub>3</sub>
0	x	x	x	0	0	0	0
1	0	0	0	0	0	0	0
1	0	0	1	1	0	0	0
1	0	1	0	0	0	0	0
1	0	1	1	0	1	0	0
1	1	0	0	0	0	0	0
1	1	0	1	0	0	1	0
1	1	1	0	0	0	0	0
1	1	1	1	0	0	0	1
 
# Demultiplexer – 1-to-4 line Demultiplexer


  
# Demultiplexer – 1-to-8 line Demultiplexer




# Encoder & Decoder

Encoders	Decoders
Encoders may have more than one input line active and may have more than one output line active at any given time	Decoders may have more than one input line active at any given time but only one output line will be active
Number of input lines is more than number of output lines	Number of output lines is more than number of input lines
Number of input lines = $2^{\text{Number of output lines}}$	Number of output lines = $2^{\text{Number of input lines}}$
Encoder is logic device used to create binary code for given decimal input	Decoder is logic device used to decode binary input to give decimal output


# Decimal to BCD Encoder

Input	Output			
Decimal digit	$B_3$	$B_2$	$B_1$	$B_0$
$D_0$	0	0	0	0
$D_1$	0	0	0	1
$D_2$	0	0	1	0
$D_3$	0	0	1	1
$D_4$	0	1	0	0
$D_5$	0	1	0	1
$D_6$	0	1	1	0
$D_7$	0	1	1	1
$D_8$	1	0	0	0
$D_9$	1	0	0	1

# Decimal to BCD Encoder – IC 7447

 

# Decimal to BCD Encoder


 


# BCD to 7 – segment Decoder

- A digital display that consists of seven LED segments is commonly used to display decimal numerals in digital systems. Most familiar examples are electronic calculators and watches where one 7-segment display device is used for displaying one numeral 0 through 9.
- For using this display device, the data has to be converted from some binary code to the code required for the display. Usually, the binary code used is natural BCD.



# BCD to 7 – segment Decoder

  

# BCD to 7 – segment Decoder – Truth Table

Decimal digit displayed	Inputs				Outputs							
	<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>a</i>	<i>b</i>	<i>c</i>	<i>d</i>	<i>e</i>	<i>f</i>	<i>g</i>	
0	0	0	0	0	1	1	1	1	1	1	0	
1	0	0	0	1	0	1	1	0	0	0	0	
2	0	0	1	0	1	1	0	1	1	0	1	
3	0	0	1	1	1	1	1	1	0	0	1	
4	0	1	0	0	0	1	1	0	0	1	1	
5	0	1	0	1	1	0	1	1	0	1	1	
6	0	1	1	0	0	0	1	1	1	1	1	
7	0	1	1	1	1	1	1	0	0	0	0	
8	1	0	0	0	1	1	1	1	1	1	1	
9	1	0	0	1	1	1	1	0	0	1	1	

# BCD to 7 – segment Decoder – K-map

$CD \backslash AB$	00	01	11	10
00	1	0	×	1
01	0	1	×	1
11	1	1	×	×
10	1	0	×	×

$CD \backslash AB$	00	01	11	10
00	1	1	×	1
01	1	0	×	1
11	1	1	×	×
10	1	0	×	×

$CD \backslash AB$	00	01	11	10
00	1	1	×	1
01	1	1	×	1
11	1	1	×	×
10	0	1	×	×

# BCD to 7 – segment Decoder – K-map

$AB \backslash CD$		00	01	11	10
00	1	0	×	1	
01	0	1	×	0	
11	1	0	×	×	
10	1	1	×	×	

$AB \backslash CD$		00	01	11	10
00	1	0	$\times$	1	
01	0	0	$\times$	0	
11	0	0	$\times$	$\times$	
10	1	1	$\times$	$\times$	

# BCD to 7 – segment Decoder – K-map

$AB \backslash CD$		$AB$			
		00	01	11	10
$CD$	00	1	1	×	1
	01	0	1	×	1
	11	0	0	×	×
	10	0	1	×	×

$AB \backslash CD$		00	01	11	10
00	0	1	×	1	
01	0	1	×	1	
11	1	0	×	×	
10	1	1	×	×	

# BCD to 7 – segment Decoder – K-map

$$a = \bar{B}\bar{D} + BD + CD + A$$

$$e = \bar{B}\bar{D} + C\bar{D}$$

$$b = \bar{B} + \bar{C}\bar{D} + CD$$

$$f = A + \bar{C}\bar{D} + B\bar{C} + B\bar{D}$$

$$c = B + \bar{C} + D = \overline{\bar{B}\bar{C}\bar{D}}$$

$$g = A + B\bar{C} + \bar{B}C + C\bar{D}$$

$$d = \bar{B}\bar{D} + C\bar{D} + \bar{B}C + B\bar{C}D$$